



Revision Sheets #03: ADC and DAC converters

1. What is **not** part of the main components in a typical A/D board?
 - a. Sensors
 - b. Input multiplexer and Input signal amplifier
 - c. Sample and hold circuit
 - d. A/D converter (ADC)
2. What is part of the main components of a typical A/D board?
 - a. Input signal amplifier
 - b) Sample and hold circuit
 - c. FIFO buffer and Timing system
 - d) Sensors
 - e) a, b, and c
3. The use of eliminates the need for a signal amplifier and an A/D converter for each input channel.
 - a) variable gain amplifier
 - b) Sample and Hold
 - c) Multiplexer
 - d) Switch
4. The use of multiplexers in A/D data acquisition boards:
 - a. Higher the cost of the board.
 - b. Limit the number of inputs.
 - c. Decrease the overall performance.
 - d. Increase the overall performance
5. What is not a plug-in data acquisition board?
 - a) Analog input (A/D)
 - b) Expansion I/O
 - c) Digital I/O
 - d) Counter/timer I/O
6. The main factor (s) in selecting an ADC (is/are)
 - a) Conversion time
 - b) Both A and C
 - c) Resolution
 - d) none of
7. Which of the following does not influence the ADC step size?
 - a) V_{ref}
 - b) Resolution
 - c) DOUT
 - d) All of the above
8. Given a step size of 11.5 mV for a 9-bit ADC, then V_{ref} equals
 - a) 5.888 V
 - b) 2.560 V
 - c) 2.944
 - d) 2.246
9. Consider an 8-bit ADC with $V_{ref}=5$. The step size is
 - a) 19.53 mV
 - b) 12.80 mV
 - c) 6.25 mV
 - d) 5.12 mV
10. Consider an 8-bit ADC with $V_{ref}=5$ and input voltage of 1.7 V. The DOUT in decimal is
 - a) 87
 - b) 132
 - c) 272
 - d) 332

Ans: 1.A, 2.E, 3.C, 4.C,5.B, 6.B,7.C,8.A ,9.A,10.A