

ADC:

Analog to Digital Converter and Sensor Interfacing

DAC:

Digital to Analog Converter

π


Introduction

- A wide range of plug-in data acquisition and control boards currently on the market are now available, used as multi-purpose plug-in data acquisition boards.
- Examples of these plug-in boards are:
 - Analog input (A/D) boards
 - Analog output (D/A) boards
 - Digital I/O boards
 - Counter/timer I/O boards

A/D boards (ADC)

- Analog input (A/D) boards convert analog voltages from external signal sources into a digital format, which can be interpreted by the host computer.
- The functional diagram of a typical A/D board is shown in figure below and comprises the following main components:
 - Input channel sample and hold circuits (for simultaneous sampling)
 - Input multiplexer
 - Input signal amplifier
 - Sample and hold circuit
 - A/D converter (ADC)
 - FIFO buffer
 - Timing system
 - Expansion bus interface

A/D boards

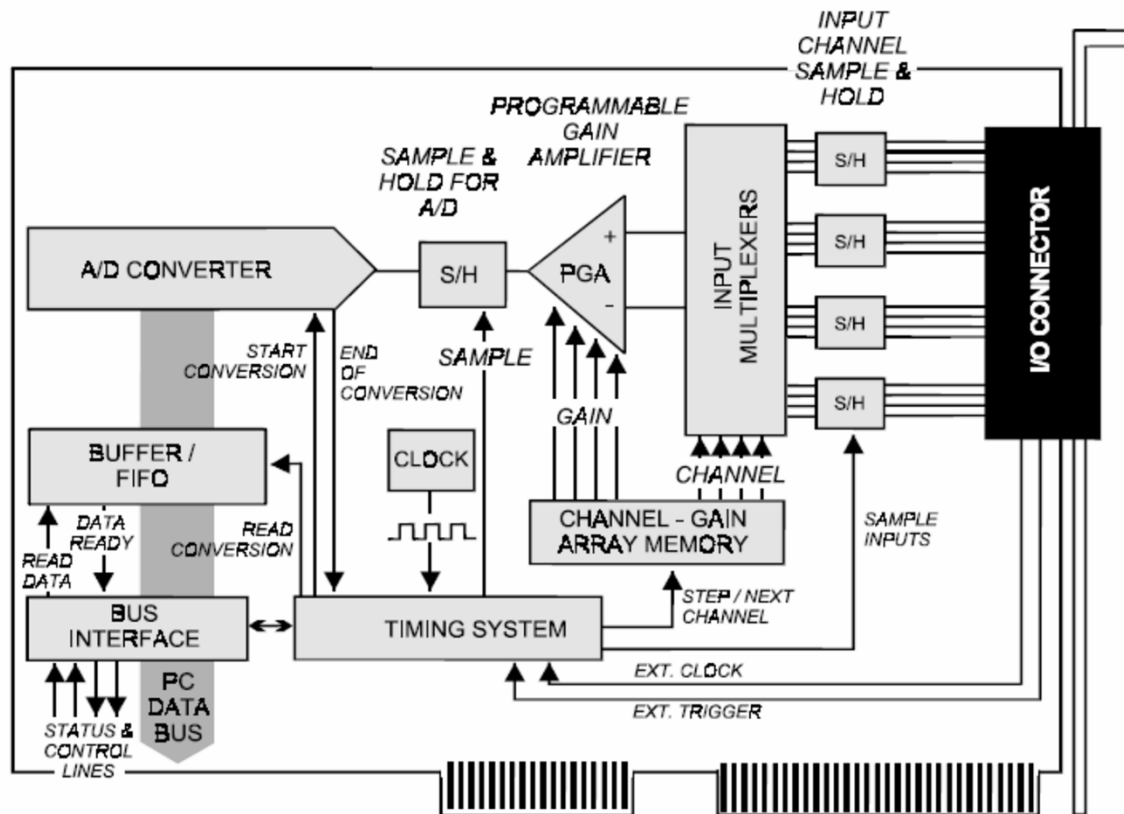



A/D boards (ADC)

A/D converters

- Analog-to-digital converters (A/D converters, ADCs) measure an analog input voltage and convert this into a digital output format.
- The main types of A/D converters used are:
 - Successive approximation A/D converter
 - Flash A/D converters
 - Integrating A/D converters



ADC Devices



- ADCs are among the most widely used devices for data acquisition and sensor interfacing.
- Digital computers use binary (discrete) values,
 - but in the physical world everything is analog (continuous).
 - Temperature, pressure (wind or liquid), humidity, and velocity...
- A physical quantity is converted to electrical (voltage, current) signals using a device called a transducer.
- Transducers used to generate electrical outputs are also referred to as **sensors**.
- Sensors for temperature, velocity, pressure, light, and many others produce an output that is voltage (or current).
- ADC translates the analog signals to digital numbers.
 - ADC takes the magnitude of the voltage and converts it to a binary value representing the magnitude.






ADC Characteristics: Resolution

- ADC has n-bit resolution,
 - where n can be 8, 10, 12, 16, or even 24 bits.
- Higher-resolution ADCs provide a smaller step size, where step size is the smallest change that can be discerned by an ADC.
- Some widely used resolutions for ADCs are shown in the Table.
- Although the resolution of an ADC chip is fixed in its Design
 - we can control the step size with the help of what is called Vref.

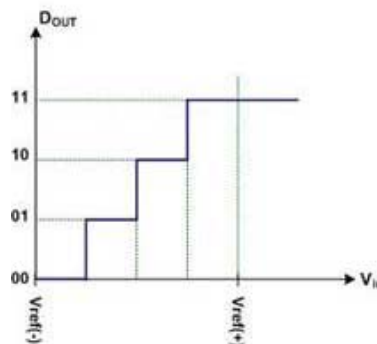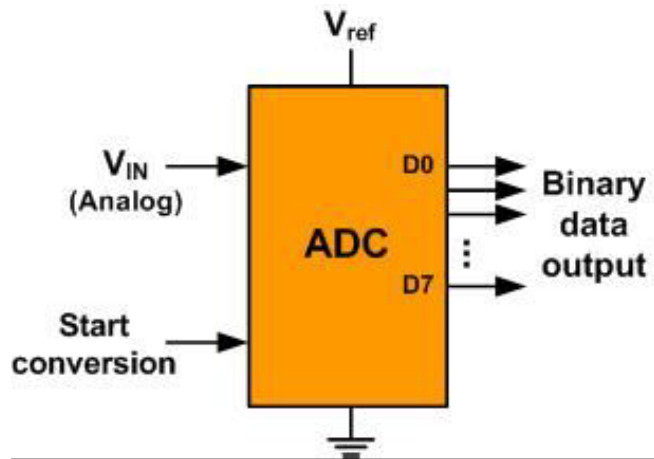

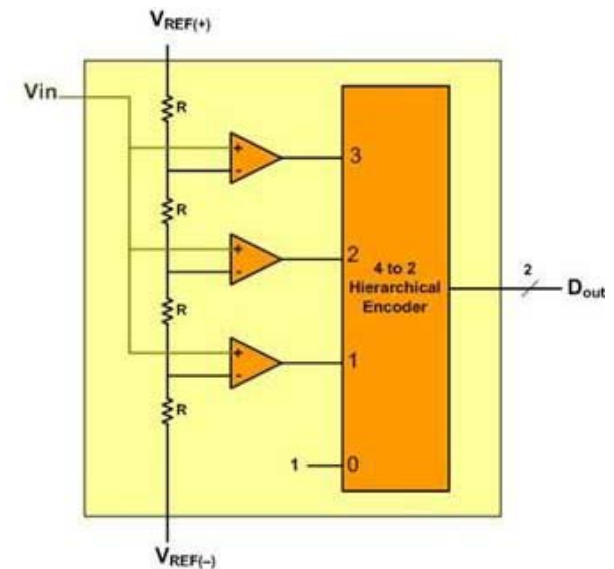(a) The Relationship between V_{in} and D_{out}



(b) The internal block diagram of a simple 2-bit ADC



ADC Characteristics: Vref

- Vref is an input to the ADC used for the reference voltage.
- Vref along with the resolution of the ADC chip, determine the step size.
- For an 8-bit ADC, the step size is $V_{ref} / 256$.
- For example, if the analog input range needs to be 0 to 4 volts,
 - Vref is connected to 4 volts.
 - That gives $4 \text{ V} / 256 = 15.62 \text{ mV}$ for the step size of an 8-bit ADC.
- In another case, if we need a step size of 10 mV for an 8-bit ADC,
 - then $V_{ref} = 2.56 \text{ V}$, because $2.56 \text{ V} / 256 = 10 \text{ mV}$.

$V_{ref} \text{ (V)}$	$V_{in} \text{ Range (V)}$	Step Size (mV)
5.00	0 to 5	$5 / 256 = 19.53$
4.00	0 to 4	$4 / 256 = 15.62$
3.00	0 to 3	$3 / 256 = 11.71$
2.56	0 to 2.56	$2.56 / 256 = 10$
2.00	0 to 2	$2 / 256 = 7.81$
1.28	0 to 1.28	$1.28 / 256 = 5$
1.00	0 to 1	$1 / 256 = 3.90$
<i>Note: In an 8-bit ADC, step size is $V_{ref}/256$</i>		

n-bit	Number of steps	Step size
8	256	$5\text{V} / 256 = 19.53 \text{ mV}$
10	1024	$5\text{V} / 1024 = 4.88 \text{ mV}$
12	4096	$5\text{V} / 4096 = 1.2 \text{ mV}$
16	65,536	$5\text{V} / 65,536 = 0.076 \text{ mV}$
<i>Note: $V_{ref} = 5\text{V}$</i>		




ADC Characteristics: Conversion time

- Conversion time is major factor in selecting an ADC, in addition to resolution.
- Conversion time is defined as:
 - the time it takes the ADC to convert the analog input to a digital number.
- The conversion time is dictated by:
 - the clock source connected to the ADC
 - the method used for data conversion
 - technology used in the fabrication of the ADC.
- Start conversion and end-of-conversion signals
 - For the conversion to be controlled by the CPU, there are needs for:
 - start conversion (**SC**) and
 - end-of-conversion (**EOC**) signals.
 - When **SC** is activated, the ADC starts converting the analog input value of V_{in} to a digital number.
 - The amount of time it takes to convert varies depending on the conversion method.
 - When the data conversion is complete, the end-of-conversion (**EOC**) signal notifies the CPU that the converted data is ready to be picked up.




ADC Characteristics: Digital data output

- In an 8-bit ADC we have an 8-bit digital data output of D0-D7
- To calculate the output voltage, we use the following formula:
 - $D_{OUT} = V_{IN} / \text{StepSize}$
 - where D_{out} = digital data output (in decimal), V_{in} = analog input voltage,
 - step size (resolution) is the smallest change, which is $V_{ref}/256$ for an 8-bit ADC.
- Ex: simple 2-bit ADC. In the circuit,
 - the voltage between $V_{ref}(+)$ and $V_{ref}(-)$ is divided into 4.
 - As a result, the step size is $(V_{ref}(+) - V_{ref}(-)) / 4$.

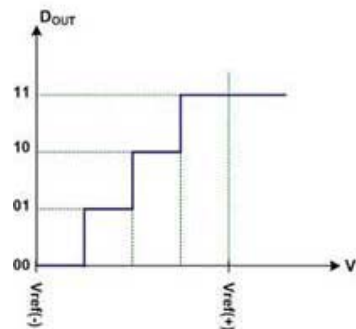

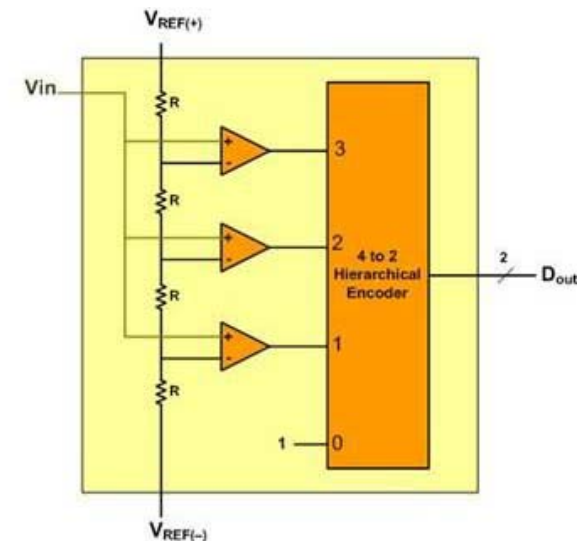(a) The Relationship between V_{in} and D_{out}



(b) The internal block diagram of a simple 2-bit ADC





ADC Characteristics: Digital data output

- Ex2: given 8-bit ADC and $V_{ref} = 2.56 \text{ V}$.
 - Calculate the D0-D7 output if the analog input is:
 - (a) 1.7 V, and (b) 2.1 V.
- Solution:
 - step size is $2.56/256 = 10 \text{ mV}$, we have the following.
 - (a) $DOUT = 1.7\text{V}/10 \text{ mV} = 170$ in decimal,
 - which gives us 10101010 in binary for D7-D0.
 - (b) $DOUT = 2.1\text{V}/10 \text{ mV} = 210$ in decimal,
 - which gives us 11010010 in binary for D7-D0



Parallel versus serial ADC


- ADC chips are either parallel or serial.
- In parallel ADC,
 - binary data is sent out with 8 or more pins.
- in serial ADC
 - we have only one pin for data out.
- The D0-D7 data pins of the 8-bit ADC provide an 8-bit parallel data path between the ADC chip and the CPU.
- Since space is a critical issue,
 - serial devices such as the serial ADC are becoming widely used.
- ADC0848 is an example of a parallel ADC with 8 pins for data output
- MAX1112 is an example of a serial ADC with a single pin for Dout.
- Analog Input Channels:
 - Typically, ADC chips has 2, 4, 8, or even 16 channels on a single chip.

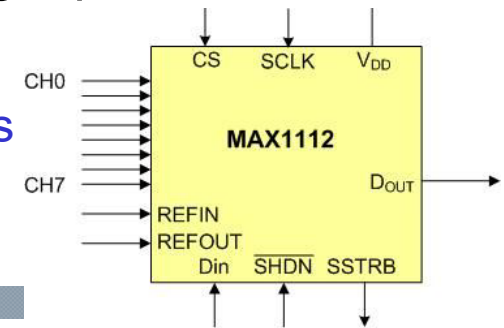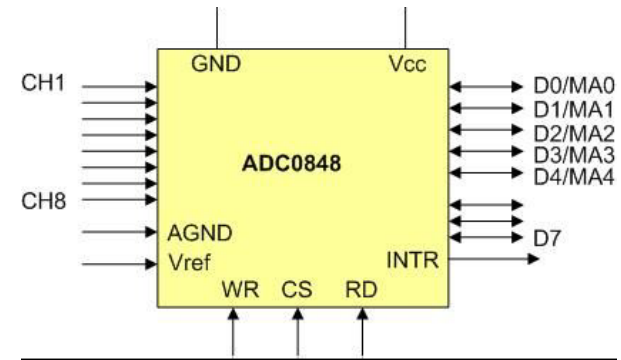



Successive Approximation ADC


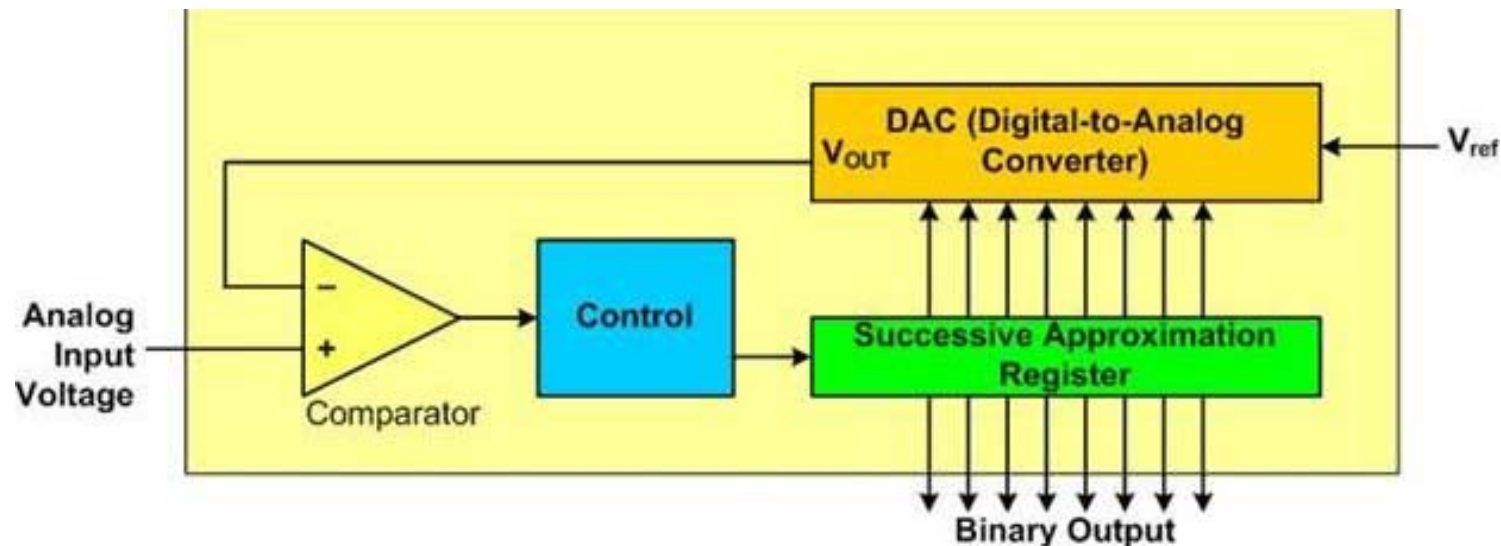
- Successive Approximation is a widely used method of converting an analog input to digital output.
- Allows high sampling rates and high resolution
- It has three main components:
 - (a) successive approximation register (SAR),
 - (b) comparator
 - (c) control unit.






Successive Approximation ADC

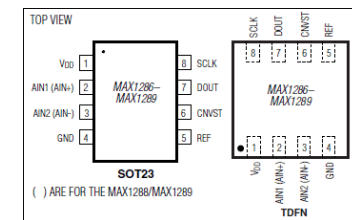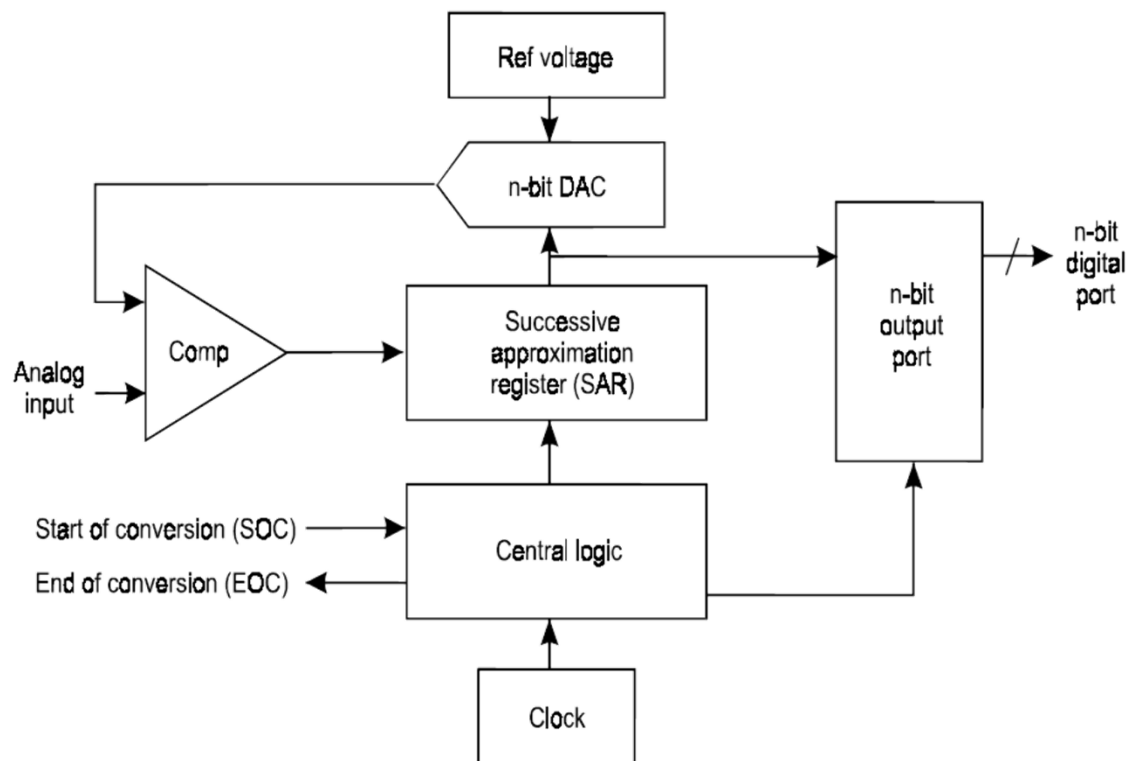- The functional diagram of an n-bit successive approximation A/D converter is shown in Figure.
- Generally speaking, an n-bit SAR ADC will require N comparison periods.




MAX1288/MAX1289
8-bit A/D

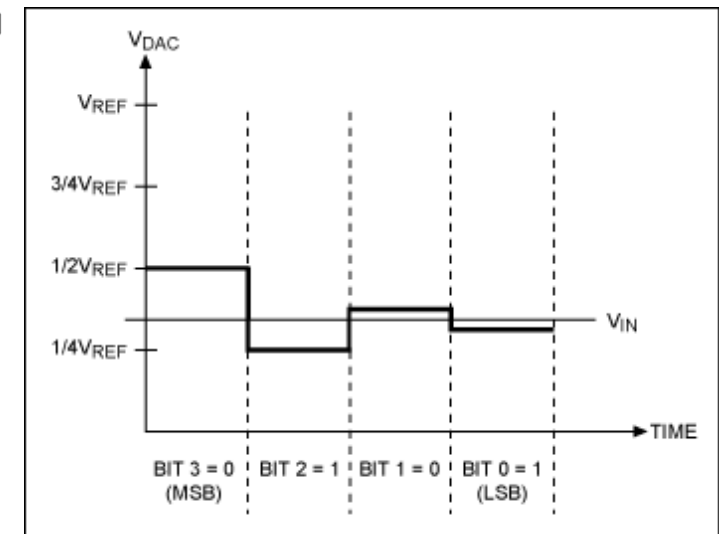



A/D boards (ADC)

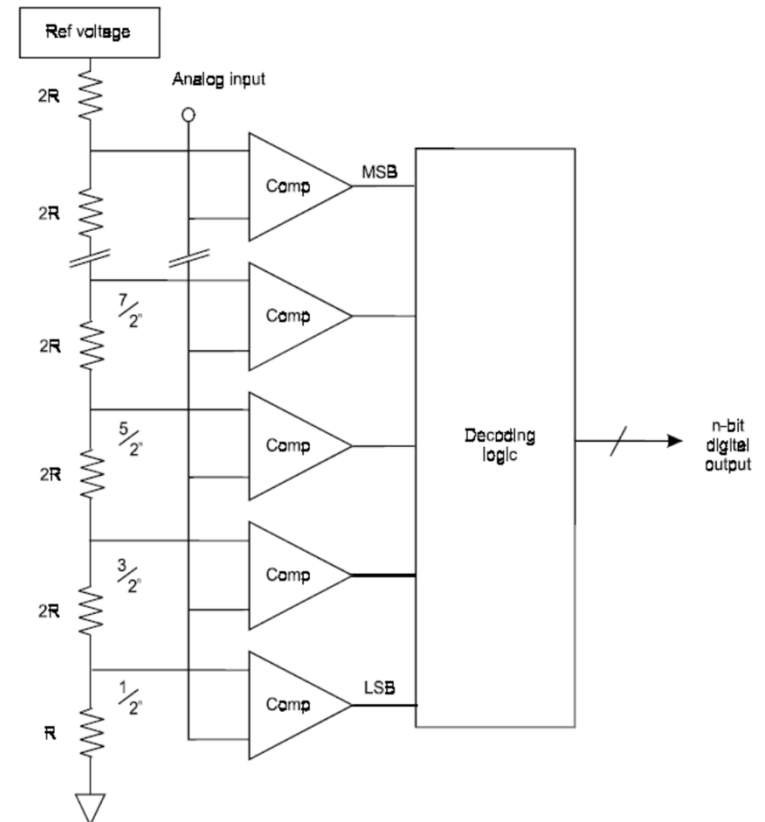- **Flash A/D converters**
- Fastest available ADC, operating at speeds up to few GHz.
- Used where extremely high speeds of conversion are required with lower resolution, for example, 8-bits.
- Figure shows the functional diagram of an n -bit flash A/D converter.
- Requires $2^n - 1$ parallel comparators.
- Found in high speed applications such as digital oscilloscopes, DSP and real-time.






A/D boards (ADC)

■ Integrating ADC

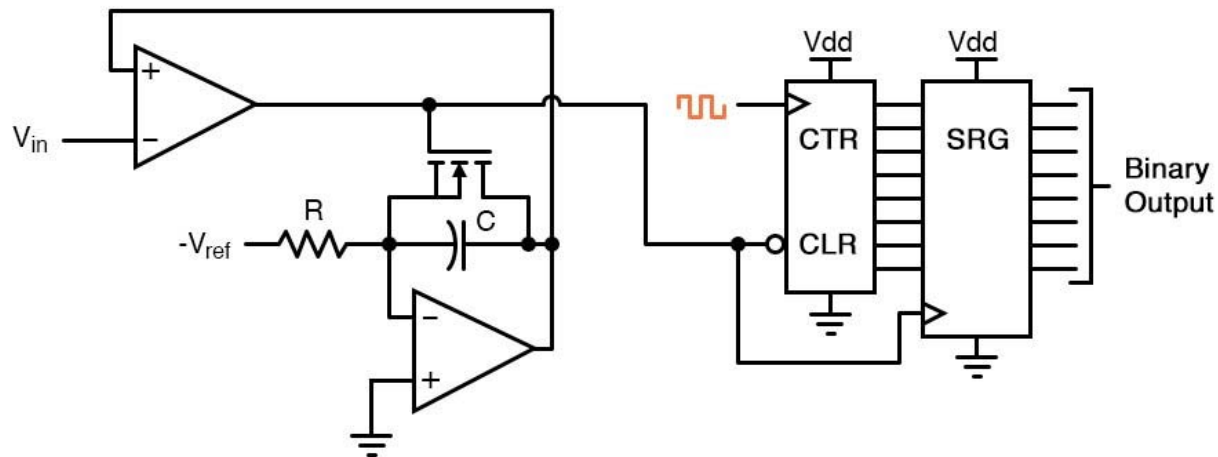- Integrating analog-to-digital converters (ADCs) provide high resolution analog-to-digital conversions, with good noise rejection. These ADCs are ideal for digitizing low bandwidth signals, and are used in applications such as digital multi-meters and panel meters.



Basic integrator of a single-slope integrating ADC



Sampling rate and the Nyquist theorem

Sampling rate and the Nyquist theorem


- How fast should the A/D board sample the data to be able to represent and reconstruct the input signal accurately.

Nyquist's theorem

Nyquist's sampling theorem states that:

*“An analog band-limited signal that has no spectral components at or above a frequency of f Hz can be uniquely represented by samples of its values spaced at uniform intervals that are no more than $\frac{1}{2} * f$ seconds apart or sampled at a frequency of no less than $2 * f$ Hz.”*

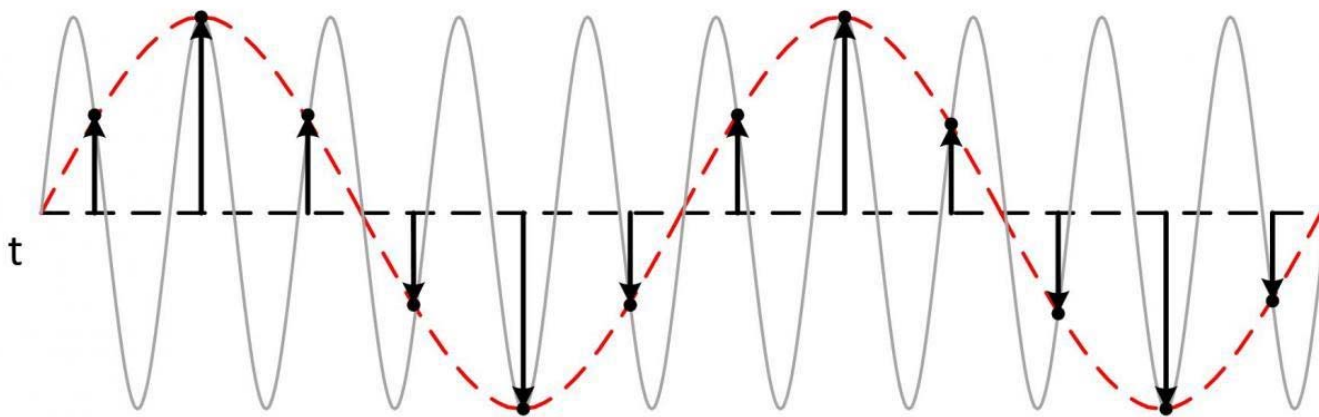- The max. sampling period, $T=1/(2*f)$, is known as the Nyquist interval, while the min. sampling frequency, $2*f$, is known as the *Nyquist sampling frequency*, or *rate*.





Digital-to-Analog (DAC) converter

- D/A boards (DAC)
- Convert digital signals from a host computer into an analog format for use by external devices such as actuators in controlling or stimulating a system or process.
- Digital to analog converters (D/A converters or DACs) accept an n-bit parallel digital code as input and provide an analog current or voltage as output.
- The primary output value is a current, however, this is easily converted to a voltage using an operational amplifier.




Digital-to-Analog (DAC) converter

- The digital-to-analog converter (DAC) is a device widely used to convert digital signals to analog signals.
- Two methods of making a DAC:
 - binary weighted and R/2R ladder.
- The vast majority of integrated circuit DACs, including the DAC0808, use the R/2R method
 - It can achieve a much higher degree of precision.
- The first criterion for selecting a DAC is:
 - its resolution, which is a function of the number of bits of the digital input.
 - The common ones are 8, 10, and 12 bits.
- The number of digital input bits decides the resolution of the DAC
 - since the number of analog output levels is equal to 2^n , where n is the number of digital input bits.
 - Therefore, the 8-bit DAC such as the DAC0808 provides 256 discrete voltage (or current) levels of output.



D/A boards (DAC)

- *Binary Weighted Resistor D/A converters*
- This method creates an output current, I_T , which is the summation of the weighted currents from each of the parallel transistor sources; the current contributed by each transistor set by the resistances R , $2R$, $4R$, $8R$, etc.
- The output is $V_0 = -I_T R/2$ the output voltage is directly proportional to the voltage reference according to the equation $V_0 = V_{REF} (B_0 2^{-1} + B_1 2^{-2} \dots + B_{n-1} 2^{n-1})$

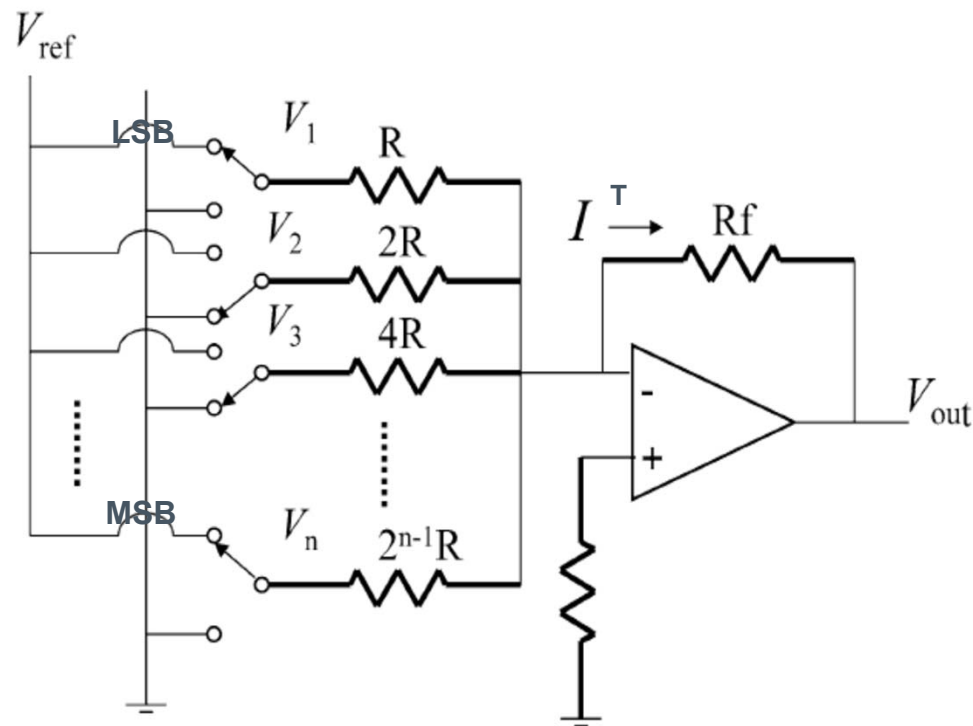




D/A boards (DAC)

R-2R ladder D/A converters

- A D/A converter which uses resistors of only two values, R and $2R$.
- The DAC produces an output current I_p proportional to the input code and the voltage reference source.
- The output is given by:

$$V_o = -V_R 2^{-n} \sum_{i=0}^{n-1} a_i 2^i; \text{ where } a_i \in \{0, 1\}$$

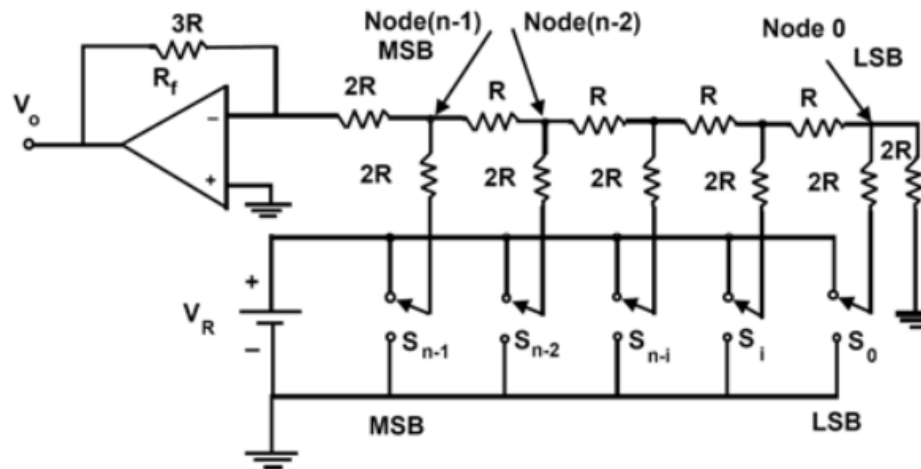- The output voltage at node $n-1$ is: $V_{n-1} = V_R/3$
- The main advantages, are
 - easy matching of resistances (R or $2R$),
 - constant and low resistance can be used, thus ensuring high-speed.





D/A boards (DAC)

Parameters of D/A converters

- Resolution
 - Output for 1bit change
 - The greater the number of input bits the smoother the output voltage
- Output range
 - Current
 - Voltage
- Input data code
 - binary, binary offset, two's complement, BCD, arbitrary, etc



DAC connection to the MCU

